

## TB6552FNG/FTG Usage considerations

### **Summary**

The TB6552FNG/FTG is a dual H- bridge driver for DC brush motor. Modes of CW, CCW, Short brake, and Stop mode are selectable and the direct PWM drive is available.

<p>This is a reference. Please do not determine the final equipment design by this material.</p>
--

## Contents

Summary.....	1
1. Power Supply Voltage .....	3
2. Output Current.....	3
3. Control input.....	3
4. PWM operation.....	5
5. Protect circuit.....	5
6. Application Circuit.....	6
7. Calculation of power dissipation .....	7
8. Others .....	7
Notes on Contents.....	8
IC Usage Considerations.....	8
Notes on handling of ICs .....	8
Points to remember on handling of ICs.....	9
RESTRICTIONS ON PRODUCT USE.....	10


## 1. Power Supply Voltage

(1) Operation power supply voltage

Characteristic	Symbol	Supply voltage	Unit
Supply voltage	V <sub>CC</sub>	2.7 to 5.5	V
	V <sub>M</sub>	2.5 to 13.5	V

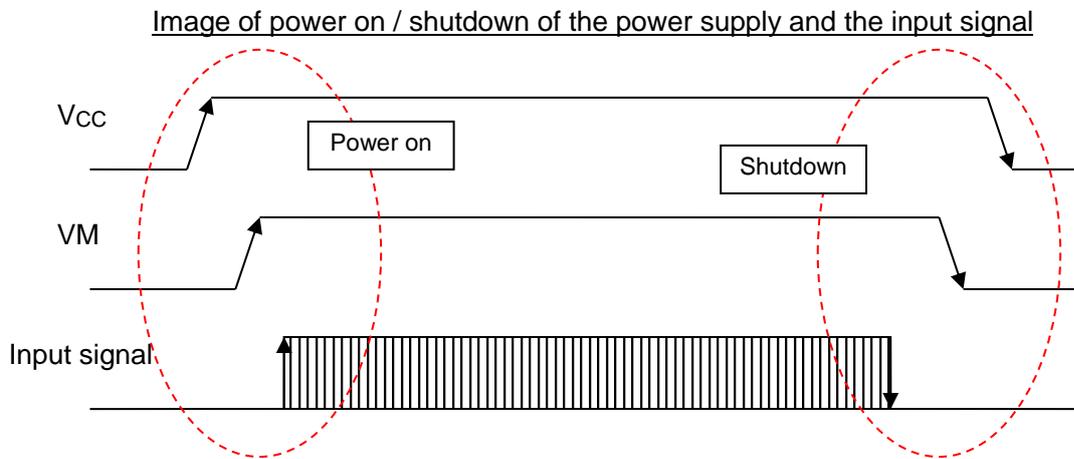(2) Power on / Shut down

- ① Please apply the power supply of VM after the power of VCC is turned on.  
(Input the input signal after the power of VCC is turned on and settled.)
- ② Please shut down the power supply of VCC after turning off the input signal, shutting down the VM, and confirming the voltage decreases enough.



In powering on and shutting down, ASTBY or BSTBY should be set to low level (Standby mode) to avoid the error in supplying V<sub>CC</sub>.

## 2. Output Current

Absolute maximum rating is 1 A (peak). It must not be exceeded, even for a moment. Average tolerant current is limited by total dissipation. Recommended operation range is 0.8 A or less. Pay attention not to exceed the dissipation in using the IC.

## 3. Control input

Please input each signal after V<sub>CC</sub> is tuned on.  
Input voltage is TTL level (0.8 to 2 V) compatible.

- (1) IN1 (AIN1 for Ach, BIN1 for Bch), IN2 (AIN2 for Ach, BIN2 for Bch), signal input  
Output mode can be chosen by IN1 or IN2 input.  
Input signal of 3 V line can control the IC when V<sub>IN</sub> (H) is 2 V and V<sub>IN</sub> (L) is 0.8 V.  
Pull down resistance of 100 kΩ (typ.) is incorporated.

(2) Standby input

All output transistors are off by setting STBY (ASTBY for Ach, BSTBY for Bch) pin to low level (Standby mode).

Input signal of 3 V line can control the IC when VIN (H) is 2 V and VIN (L) is 0.8 V.

Pull down resistance of 100 kΩ (typ.) is incorporated. IC moves to standby mode when input pin is open.

(3) Direct PWM signal input

PWM (APWM for Ach, BPWM for Bch) pin is a direct PWM signal input pin.

**Direct PWM function (Common for channel A and B)**


Input				Output		
IN1	IN2	STBY	PWM	O1	O2	Mode
H	H	H	H	L	L	Short brake
			L			
L	H	H	H	L	H	CW/CCW
			L	L	L	Short brake
H	L	H	H	H	L	CCW/CW
			L	L	L	Short brake
L	L	H	H	OFF (High impedance)		Stop
			L			
H/L	H/L	L	H	OFF (High impedance)		Standby
			L			

## 4. PWM operation

During PWM operation, normal operation and short brake operation are repeated.

If the upper and lower power transistors in the output circuit were ON at the same time, a shoot-through current would be produced. To prevent this current from being produced, a dead time of 300 ns (design target value) is provided in the IC when either of the transistors changes from ON to OFF, or vice versa.

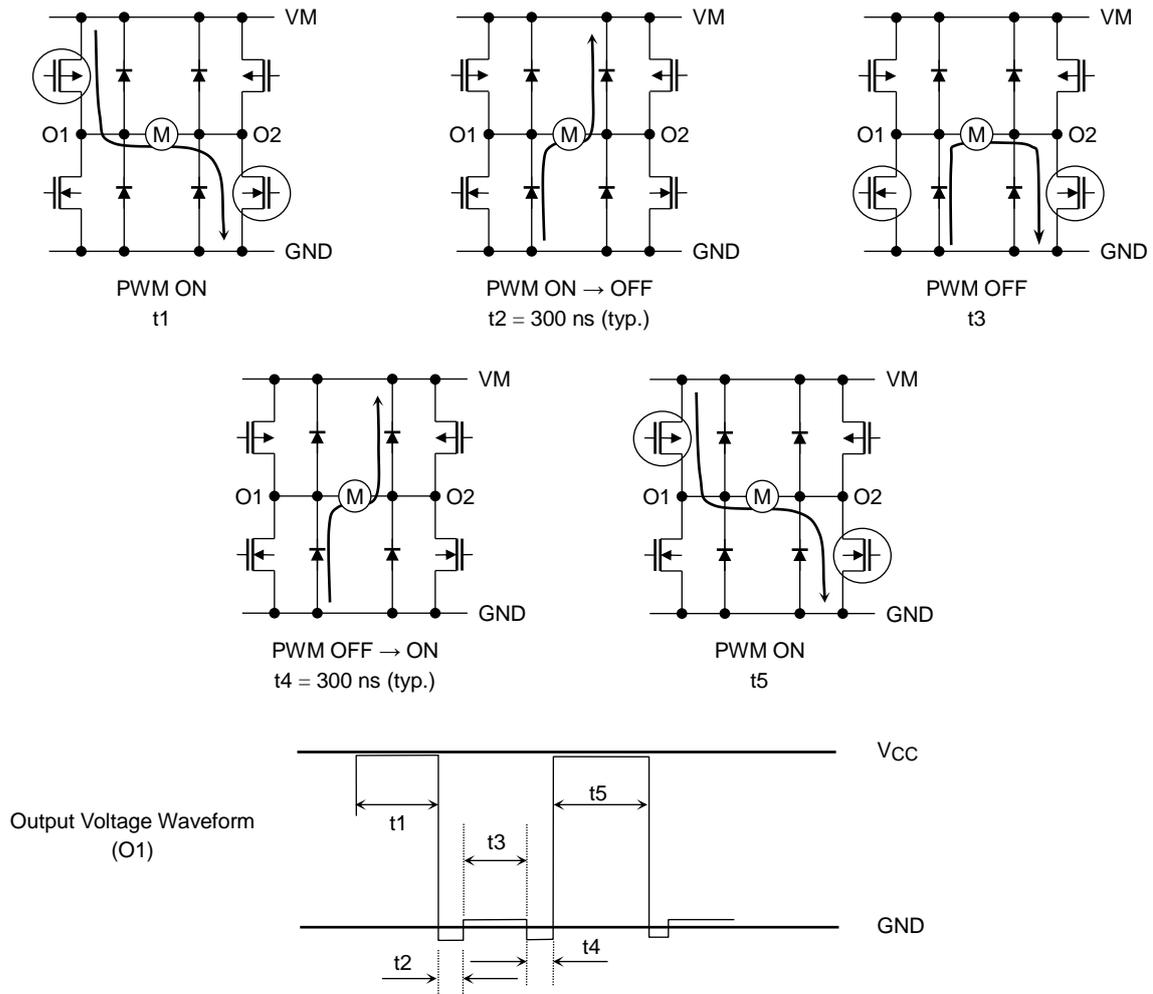Therefore, synchronous rectification PWM control is realized without an OFF time being inserted by external input. Note that a dead time is also provided in the IC at the time of transition between CW and CCW or between CW (CCW) and short brake mode, thereby eliminating the need for an OFF time.



## 5. Protect circuit


This IC includes the functions below but it is not intended to protect ICs under all circumstances. Be sure to use the IC within the rating. If a short circuit takes place between output pins or if an output pin is connected to the voltage source or ground directory, a heavy current temporarily flows though the IC. It might destroy the IC.

<Thermal shutdown circuit>

All outputs turn off when junction temperature exceeds 170 °C (typ.).

It has also temperature hysteresis of 20 °C (typ.). They recover when junction temperature decreases to 150 °C.

**6. Application Circuit**

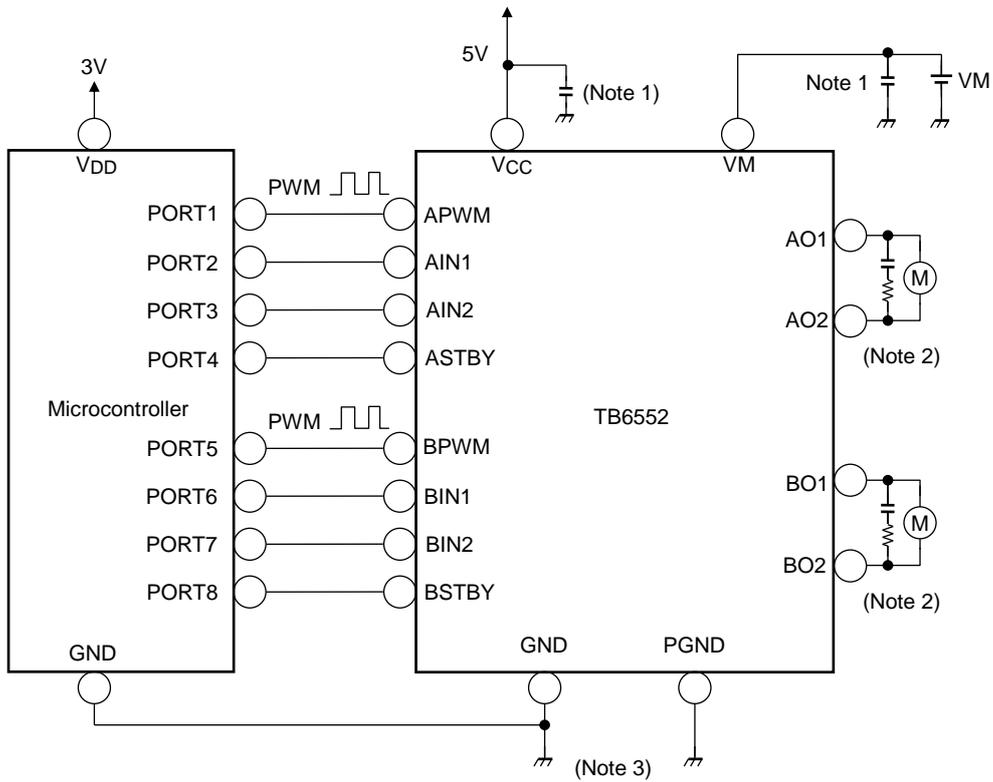

Note1: Connect the capacitor between V<sub>CC</sub> (VM) and GND as near the IC as possible.

Note2: When connecting the motor pins through the capacitor for reducing noise, connect a resistor to the capacitor to limit the charge current.

Note3: Avoid using common impedance for GND and PGND.

\*) Capacitor for supply pin  
 <Recommended value>

Capacitor	Recommended values	Remarks
C1 (Between V <sub>CC</sub> and GND)	10 μF to 33 μF	Electrolytic capacitor
	0.001 μF to 0.1 μF	Ceramic capacitor
C2 (Between VM and GND)	10 μF to 100 μF	Electrolytic capacitor
	0.001 μF to 0.1 μF	Ceramic capacitor

## 7. Calculation of power dissipation

Power dissipation is calculated by the formula below.  
<PWM Duty = 100%>

$$P = V_{CC} \times I_{CC} + I_o^2 \times R_{on} \text{ (upper + lower)}$$

When the ambient temperature is high, the dissipation becomes low. Design the radiation taking enough margins by applying Pd - Ta property data.




The relation between ambient temperature and junction temperature is calculated by the formula below. Be sure to set the junction temperature 150 °C or less.

$$T_j = P \times R_{th} (j-a) + T_a$$

\* Rth (j-a): Heat resistance between junction and ambient temperature

\* Ta: Ambient temperature

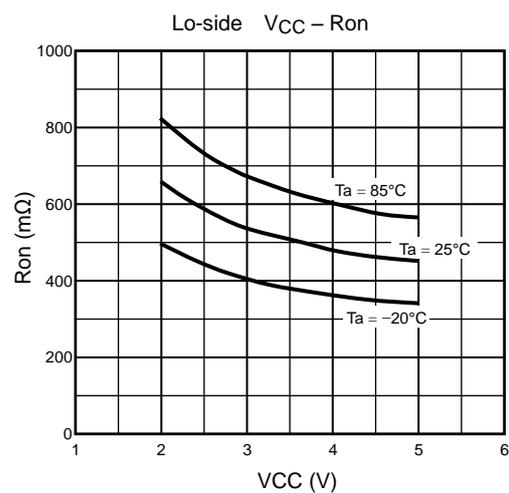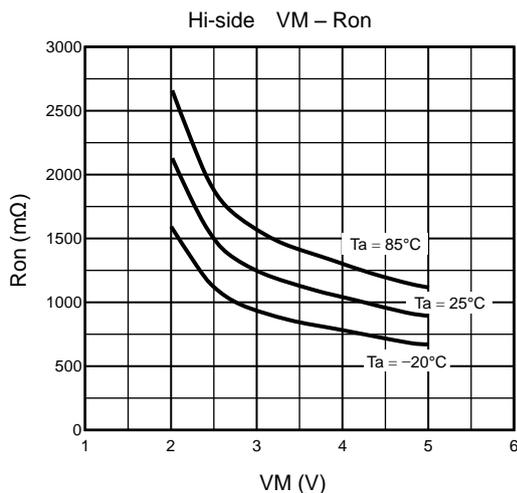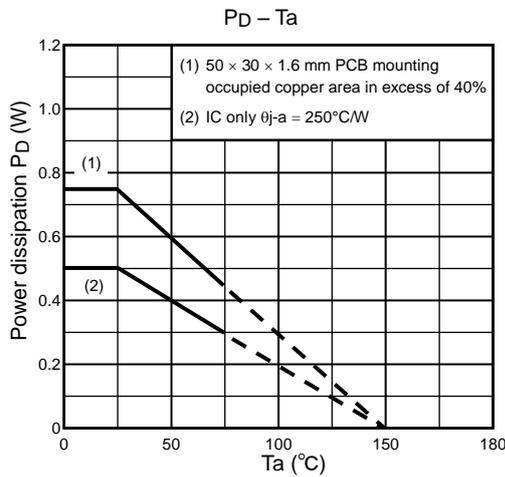Pay attention that Rth (j-a) depends on the usage circumstances (ex. mounted board).  
(Reference data of transient heat resistance in boarding only IC or constant conditioned IC is shown below.)



## 8. Others

The TB6552FNG/FTG has a CMOS device in the limit circuit and has a LDMOS (Pch/Nch) device in output circuit.

Generally, MOS devices are highly sensitive to electrostatic discharge. When handling them, ensure that the environment is protected against electrostatic discharge.

## Notes on Contents

1. Block Diagrams  
Some of the functional blocks, circuits, or constants in the block diagram may be omitted or simplified for explanatory purposes.
2. Equivalent Circuits  
The equivalent circuit diagrams may be simplified or some parts of them may be omitted for explanatory purposes.
3. Timing Charts  
Timing charts may be simplified for explanatory purposes.
4. Application Circuits  
The application circuits shown in this document are provided for reference purposes only. Thorough evaluation is required, especially at the mass production design stage.  
Toshiba does not grant any license to any industrial property rights by providing these examples of application circuits.
5. Test Circuits  
Components in the test circuits are used only to obtain and confirm the device characteristics. These components and circuits are not guaranteed to prevent malfunction or failure from occurring in the application equipment.

## IC Usage Considerations

### Notes on handling of ICs

- (1) The absolute maximum ratings of a semiconductor device are a set of ratings that must not be exceeded, even for a moment. Do not exceed any of these ratings.  
Exceeding the rating(s) may cause the device breakdown, damage or deterioration, and may result injury by explosion or combustion.
- (2) Use an appropriate power supply fuse to ensure that a large current does not continuously flow in case of over current and/or IC failure. The IC will fully break down when used under conditions that exceed its absolute maximum ratings, when the wiring is routed improperly or when an abnormal pulse noise occurs from the wiring or load, causing a large current to continuously flow and the breakdown can lead smoke or ignition. To minimize the effects of the flow of a large current in case of breakdown, appropriate settings, such as fuse capacity, fusing time and insertion circuit location, are required.
- (3) If your design includes an inductive load such as a motor coil, incorporate a protection circuit into the design to prevent device malfunction or breakdown caused by the current resulting from the inrush current at power ON or the negative current resulting from the back electromotive force at power OFF. IC breakdown may cause injury, smoke or ignition.  
Use a stable power supply with ICs with built-in protection functions. If the power supply is unstable, the protection function may not operate, causing IC breakdown. IC breakdown may cause injury, smoke or ignition.
- (4) Do not insert devices in the wrong orientation or incorrectly.  
Make sure that the positive and negative terminals of power supplies are connected properly. Otherwise, the current or power consumption may exceed the absolute maximum rating, and exceeding the rating(s) may cause the device breakdown, damage or deterioration, and may result injury by explosion or combustion.  
In addition, do not use any device that is applied the current with inserting in the wrong orientation or incorrectly even just one time.

**Points to remember on handling of ICs****(1) Thermal Shutdown Circuit**

Thermal shutdown circuits do not necessarily protect ICs under all circumstances. If the thermal shutdown circuits operate against the over temperature, clear the heat generation status immediately.

Depending on the method of use and usage conditions, such as exceeding absolute maximum ratings can cause the thermal shutdown circuit to not operate properly or IC breakdown before operation.

**(2) Heat Radiation Design**

In using an IC with large current flow such as power amp, regulator or driver, please design the device so that heat is appropriately radiated, not to exceed the specified junction temperature ( $T_j$ ) at any time and condition. These ICs generate heat even during normal use. An inadequate IC heat radiation design can lead to decrease in IC life, deterioration of IC characteristics or IC breakdown. In addition, please design the device taking into consideration the effect of IC heat radiation with peripheral components.

**(3) Back-EMF**

When a motor rotates in the reverse direction, stops or slows down abruptly, a current flow back to the motor's power supply due to the effect of back-EMF. If the current sink capability of the power supply is small, the device's motor power supply and output pins might be exposed to conditions beyond absolute maximum ratings. To avoid this problem, take the effect of back-EMF into consideration in system design.

## RESTRICTIONS ON PRODUCT USE

- Toshiba Corporation, and its subsidiaries and affiliates (collectively "TOSHIBA"), reserve the right to make changes to the information in this document, and related hardware, software and systems (collectively "Product") without notice.
- This document and any information herein may not be reproduced without prior written permission from TOSHIBA. Even with TOSHIBA's written permission, reproduction is permissible only if reproduction is without alteration/omission.
- Though TOSHIBA works continually to improve Product's quality and reliability, Product can malfunction or fail. Customers are responsible for complying with safety standards and for providing adequate designs and safeguards for their hardware, software and systems which minimize risk and avoid situations in which a malfunction or failure of Product could cause loss of human life, bodily injury or damage to property, including data loss or corruption. Before customers use the Product, create designs including the Product, or incorporate the Product into their own applications, customers must also refer to and comply with (a) the latest versions of all relevant TOSHIBA information, including without limitation, this document, the specifications, the data sheets and application notes for Product and the precautions and conditions set forth in the "TOSHIBA Semiconductor Reliability Handbook" and (b) the instructions for the application with which the Product will be used with or for. Customers are solely responsible for all aspects of their own product design or applications, including but not limited to (a) determining the appropriateness of the use of this Product in such design or applications; (b) evaluating and determining the applicability of any information contained in this document, or in charts, diagrams, programs, algorithms, sample application circuits, or any other referenced documents; and (c) validating all operating parameters for such designs and applications. **TOSHIBA ASSUMES NO LIABILITY FOR CUSTOMERS' PRODUCT DESIGN OR APPLICATIONS.**
- **PRODUCT IS NEITHER INTENDED NOR WARRANTED FOR USE IN EQUIPMENTS OR SYSTEMS THAT REQUIRE EXTRAORDINARILY HIGH LEVELS OF QUALITY AND/OR RELIABILITY, AND/OR A MALFUNCTION OR FAILURE OF WHICH MAY CAUSE LOSS OF HUMAN LIFE, BODILY INJURY, SERIOUS PROPERTY DAMAGE AND/OR SERIOUS PUBLIC IMPACT ("UNINTENDED USE").** Except for specific applications as expressly stated in this document, Unintended Use includes, without limitation, equipment used in nuclear facilities, equipment used in the aerospace industry, medical equipment, equipment used for automobiles, trains, ships and other transportation, traffic signaling equipment, equipment used to control combustions or explosions, safety devices, elevators and escalators, devices related to electric power, and equipment used in finance-related fields. **IF YOU USE PRODUCT FOR UNINTENDED USE, TOSHIBA ASSUMES NO LIABILITY FOR PRODUCT.** For details, please contact your TOSHIBA sales representative.
- Do not disassemble, analyze, reverse-engineer, alter, modify, translate or copy Product, whether in whole or in part.
- Product shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable laws or regulations.
- The information contained herein is presented only as guidance for Product use. No responsibility is assumed by TOSHIBA for any infringement of patents or any other intellectual property rights of third parties that may result from the use of Product. No license to any intellectual property right is granted by this document, whether express or implied, by estoppel or otherwise.
- **ABSENT A WRITTEN SIGNED AGREEMENT, EXCEPT AS PROVIDED IN THE RELEVANT TERMS AND CONDITIONS OF SALE FOR PRODUCT, AND TO THE MAXIMUM EXTENT ALLOWABLE BY LAW, TOSHIBA (1) ASSUMES NO LIABILITY WHATSOEVER, INCLUDING WITHOUT LIMITATION, INDIRECT, CONSEQUENTIAL, SPECIAL, OR INCIDENTAL DAMAGES OR LOSS, INCLUDING WITHOUT LIMITATION, LOSS OF PROFITS, LOSS OF OPPORTUNITIES, BUSINESS INTERRUPTION AND LOSS OF DATA, AND (2) DISCLAIMS ANY AND ALL EXPRESS OR IMPLIED WARRANTIES AND CONDITIONS RELATED TO SALE, USE OF PRODUCT, OR INFORMATION, INCLUDING WARRANTIES OR CONDITIONS OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, ACCURACY OF INFORMATION, OR NONINFRINGEMENT.**
- Do not use or otherwise make available Product or related software or technology for any military purposes, including without limitation, for the design, development, use, stockpiling or manufacturing of nuclear, chemical, or biological weapons or missile technology products (mass destruction weapons). Product and related software and technology may be controlled under the applicable export laws and regulations including, without limitation, the Japanese Foreign Exchange and Foreign Trade Law and the U.S. Export Administration Regulations. Export and re-export of Product or related software or technology are strictly prohibited except in compliance with all applicable export laws and regulations.
- Please contact your TOSHIBA sales representative for details as to environmental matters such as the RoHS compatibility of Product. Please use Product in compliance with all applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive. **TOSHIBA ASSUMES NO LIABILITY FOR DAMAGES OR LOSSES OCCURRING AS A RESULT OF NONCOMPLIANCE WITH APPLICABLE LAWS AND REGULATIONS.**