# Bipolar Transistors Electrical and Equivalent Circuit

## Description

This document describes the electrical characteristics of bipolar transistors.

## **Table of Contents**

Description	. 1
Table of Contents	. 2
1. Transistor characteristics	.4
1.1. Device parameters	5
1.2. Circuit parameters	.11
1.3. Low-frequency, low-noise amplifiers	18
RESTRICTIONS ON PRODUCT USE	25

## List of Figures

Figure 1.1 Early's T-type equivalent circuit5
Figure 1.2 Frequency locus of a8
Figure 1.3 π-type equivalent circuit9
Figure 1.4 Circuit network using the h matrix11
Figure 1.5 Circuit network using the y matrix11
Figure 1.6 Circuit network using the S matrix12
Figure 1.7 Frequency locus of h parameters
Figure 1.8 Frequency locus of y parameters
Figure 1.9 Relationship between NF and frequency19
Figure 1.10 Noise source of transistor
Figure 1.11 Total noise voltage – Signal source resistance
Figure 1.12 NF – R <sub>g</sub> , I <sub>C</sub> (1)21
Figure 1.13 NF – R <sub>g</sub> , I <sub>C</sub> (2)
Figure 1.14 Noise figure of a multi-stage amplifier
Figure 1.15 Equivalent noise resistance of a multi-stage amplifier

### **List of Tables**

Table 1.1 List of transistor equivalent circuits	4
Table 1.2 Relationships between the parameters of the T-type and the $\pi$ -type equivalent circ	cuits
	10
Table 1.3 Interrelation of parameters	13
Table 1.4 Conversion formulas for h parameters	14
Table 1.5 Conversion formulas for y parameters	15
Table 1.6 h parameters converted using T-type equivalent circuit	16
Table 1.7 y parameters converted using T-type equivalent circuit	16
Table 1.8 Types of noise	19

## 1. Transistor characteristics

Equivalent parameters of a transistor include the device parameters closely related to its internal operation and the circuit parameters that are represented as a matrix by treating the transistor as a four-terminal network.

Equivalent circuits are also divided into small-signal and large-signal equivalent circuits, depending on the amplitude of signals to be handled. Since there are numerous equivalent circuits, circuit designers should carefully consider the scopes and limitations of their applications. Table 1.1 categorizes equivalent circuits. Chapter 1 focuses on commonly used small-signal equivalent circuits.

Transistor equivalent - circuits	Small-signal equivalent circuits (General linear circuits such as amplifiers, oscillators, modulators, and demodulators)	Device parameters	Early's T-type equivalent circuit (Common-base circuit) Giacoletto's n-type equivalent circuit (Common-collector and common-emitter circuits) Matrices showing the relationship between the input and output by voltage and current a-b matrixes g-h matrices (low frequency) y-z matrices (high frequency) Matrices showing the relationship between the input and output by power s matrices (ultra-high frequency) (transmittance coefficient and reflection coefficient indications)
	Large-signal equivalent circuits - device parameters (Nonlinear circuits such as pulse, digital, and switching circuits)		Ebers-Moll current control model Beaufoy-Sparkes charge control model Linvil density control model Other nonlinear models

#### Table 1.1 List of transistor equivalent circuits

#### 1.1. Device parameters

(1) Early's T-type equivalent circuit

Figure 1.1 shows Early's T-type equivalent circuit.



# Figure 1.1 Early's T-type equivalent circuit

(a) re: Emitter resistance

 $r_e$  is the forward-bias resistance across the base-emitter junction, which is calculated as:

$$r_{e} = \frac{k T}{q I_{E}} (\Omega) \qquad (1-1)$$

- k : Boltzmann constant ( $1.38 \times 10^{-23}$  J/ K)
- T : Absolute temperature (K)
- q : Elementary charge  $(1.602 \times 10^{-19} \text{ C})$
- $I_E$  : Emitter current (A)

At room temperature (300 K), Equation 1-1 is restated as follows when the emitter current is given in mA:

$$r_e \approx \frac{26}{I_E (mA)} (\Omega)$$
 (1-2)

(b)  $C_e$ : Emitter capacitance ( $C_{Te}+C_{De}$ )

The emitter capacitance is the sum of the depletion capacitance  $C_{Te}$  and the diffusion capacitance  $C_{De}$  in the base-emitter junction. The depletion layer capacitance in the base-emitter junction can be ignored since it is far smaller than the diffusion capacitance. The depletion layer capacitance  $C_{Te}$  and the diffusion capacitance  $C_{De}$  can be calculated using Equation 1-3 and Equation 1-4 respectively:

$$C_{Te} = A_{e} \int_{0}^{3} \frac{\frac{1}{2} \epsilon q^{n} N}{\phi_{0} - V_{b'e}} \quad (F) \quad (1-3)$$

 $A_e$ : Emitter junction area (m<sup>2</sup>)

- $\epsilon$  : Dielectric constant
- $^{n}N$  : Majority carrier density (m $^{-3})$  on the side with higher specific resistance (NPN in this case)
- $\Phi_0$ : Contact potential difference (potential barrier in thermodynamic equilibrium) (V)
- $V_{b^\prime e}\colon$  Voltage applied across the base-emitter junction (V)

$$C_{De} = \frac{q I_E W^2}{2 k T D} (F)$$
 (1-4)

- W : Base width (m)
- D : Diffusion coefficient of minority carriers in the base layer  $(m^2/s)$

#### (c) $\mu$ : Voltage feedback ratio (Early constant)

This constant due to the Early effect is a base-width modulation parameter.

$$\mu = \frac{k T d_{C}}{3 q W \left(\phi_{0} - V_{b'e}\right)} \quad (F) \quad \dots \quad (1-5)$$

 $d_{\mathsf{C}}~:~\text{Width of the collector depletion layer (m)}$ 

(d) r<sub>c</sub> : Collector resistance

This is a base-width modulation parameter, which is represented as:

$$r_{\rm C} = \frac{1}{I_{\rm E} \left(\frac{\partial \alpha}{\partial V_{\rm b'c}}\right)} \quad (\Omega) \qquad (1-6)$$

 $r_{c}$  is typically 1 to 2  $M\Omega.$ 

#### (e) Cc : Collector capacitance

As is the case with the emitter capacitance, the collector capacitance is the sum of the depletion layer capacitance  $C_{TC}$  and the diffusion capacitance  $C_{DC}$  in the collector-base junction.

The diffusion capacitance in the collector-base junction can be ignored since it is far smaller than the depletion layer capacitance. The depletion layer capacitance can be calculated as:

$$C_{TC} = A_C \sqrt[3]{\frac{\epsilon^2 q a}{\frac{12}{\phi_0 - V_{b'c}}}}$$
 (F) (1-7)

 $A_C$  : Collector junction area (m<sup>3</sup>)

a : Dopant concentration gradient  $(m^{-4})$ 

 $V_{b^\prime c}$  : Voltage applied across the base-collector junction (V)

 $C_{TC}$  is typically 1 to 10 pF.

#### (f) $\alpha$ : DC current gain

This is the only parameter of Early's T-type equivalent circuit that exhibits frequency dependence and can be calculated as:

$$\alpha = \frac{\alpha_0}{1 + j \omega C_e r_c}$$
$$f_\alpha = \frac{1}{2 \pi C_e r_e}$$

Hence:

$$\alpha = \frac{\alpha_0}{1 + j \frac{f}{f_\alpha}} \qquad (1-8)$$

 $\alpha_0$  : Value of a at low frequency

 $f_{\alpha}$  :  $\alpha$  cut-off frequency (frequency at which  $\alpha$  drops by 3 dB)

Figure 1.2 shows the frequency locus of  $\alpha$ . The measurement of  $\alpha$  reveals that the difference between theoretical and measured values increases as the frequency approaches  $f_{\alpha}$ . This is because Early's T-type equivalent circuit is based on primary approximation of physical phenomena.

 $T_{o}$  correct this error, Thomas-Moll included the excess phase parameter m in the equation:

$$\alpha = \frac{\alpha_0}{1 + j \frac{f}{f_\alpha}} e^{-j} m \frac{f}{f_\alpha}$$
(1-9)

This equation matches well with measured values at frequencies lower than  $f_{\boldsymbol{\alpha}}$ 



Figure 1.2 Frequency locus of  $\boldsymbol{\alpha}$ 

(g) r<sub>bb'</sub> : Base spreading resistance
This is the resistance from the center of the base layer to the external base terminal that contributes to the operation of a transistor and is determined by the shape and dimensions of the transistor and the specific resistance of the base layer. The comb-shaped base spreading resistance can be calculated as follows.



- $r_{bb'} \approx \frac{1}{12} \frac{\rho_B}{W} \frac{L}{Z}$  (Ω)······ (1-10)
- $\rho_B$  ~ Specific resistance of the base layer ( $\Omega {\cdot} m)$

In a common-emitter configuration, the DC current gain ( $\beta$ ) of a transistor is represented as follows using  $\pi$ -type equivalent circuit:

$$\beta = \frac{\alpha_0}{1 - \alpha_0} \left( \frac{1}{1 + j \,\omega \, C_{b'e} \, r_{b'e}} \right) = \frac{\beta_0}{1 + j \,\omega \, C_{b'e} \, r_{b'e}}$$

As is the case with  $f_{\alpha}$ , let's define the  $\beta$  cut-off frequency  $f_{\beta}$  as the frequency at which the absolute value of  $\beta$  equals  $\beta_0/\sqrt{2}$ . Then,  $f_{\beta}$  is calculated as:

(2)  $\pi$ -type equivalent circuit

Figure 1.3 shows the  $\pi$ -type equivalent circuit, which is essentially the same as the Ttype equivalent circuit described above. The  $\pi$ -type equivalent circuit differs from the Ttype equivalent circuit only in that, in principle, the parameters of the former have no frequency response.

Since the physical meaning of each parameter is easy to understand, the  $\pi$ -type equivalent circuit is widely used. To use it for circuit calculation, it is convenient to simplify the basic configuration shown in Figure 1.3, considering the frequency range.

Table 1.2 shows the relationships of the parameters of the T-type and the  $\pi$ -type equivalent circuits.



Figure 1.3  $\pi$ -type equivalent circuit

T-type equivalent circuit	$\pi$ -type equivalent circuit
C <sub>e</sub>	C <sub>b'e</sub>
$\frac{r_e}{1-\alpha_0}$	г <sub>b'e</sub>
$C_{c}$	C <sub>b</sub> ′c
$\frac{1}{r_{e}} - \frac{\mu (1 - \alpha_{0})}{r_{e}}$	1 r <sub>b'c</sub>
r <sub>e</sub> μ	r <sub>ce</sub>
$\frac{\alpha_0}{r_e}$	gm
r <sub>bb</sub> ′	Г <sub>bb</sub> ′

# Table 1.2 Relationships between the parameters of the T-type and the $\pi$ -type equivalent circuits

#### 1.2. Circuit parameters

 Matrices showing the relationships between the input and the output by voltage and current

This method regards a transistor as a four-terminal circuit network to describe it only with the electrical characteristics of its terminals irrespective of the physical characteristics of the transistor.

There are six types of matrices (a, b, g, h, y and z) that represent the relationships among the input and output voltages and currents. Of the six types, the h and y matrices are used relatively frequently.

Figure 1.4 and Figure 1.5 show the definitions of the h and y matrices. The suffixes e and b following the letters i, r, f, and o distinguish between the common-emitter and common-base configurations.



Figure 1.4 Circuit network using the h matrix



#### Figure 1.5 Circuit network using the y matrix

y<sub>r</sub>∶

Reverse transfer admittance

The parameters in the matrices have the following meanings:

- h<sub>i</sub> : Input impedance y<sub>i</sub> : Input admittance
- $h_r$ : Reverse voltage feedback ratio
- $h_f$ : Forward current gain  $y_f$ : Forward transfer admittance
- h<sub>o</sub>: Output admittance y<sub>o</sub>: Output admittance

The h matrices are often used for low-frequency regions whereas the y matrices are commonly used for high-frequency regions.

(2) Matrix showing the relationships between the input and the output by power

The S matrices (scattering matrices) are commonly used to represent the phenomena in microwave circuits such as the reflection and transmission of waves.

As the frequency limits of semiconductor devices increase, the S matrices are sometimes used to describe their circuit parameters.

Figure 1.6 shows the definitions of the S matrix.



 $\left[\begin{array}{c} b_1 \\ b_2 \end{array}\right] = \left[\begin{array}{c} S_{11} & S_{12} \\ S_{21} & S_{22} \end{array}\right] \left[\begin{array}{c} a_1 \\ a_2 \end{array}\right] = \left[\begin{array}{c} S_i & S_r \\ S_f & S_o \end{array}\right] \left[\begin{array}{c} a_1 \\ a_2 \end{array}\right]$ 

#### Figure 1.6 Circuit network using the S matrix

Each parameter has the following meaning:

- $S_{11}$  : Input reflection coefficient
- S<sub>12</sub> : Reverse transmission coefficient
- $S_{21}$  : Forward transmission coefficient
- $S_{22}$  : Output reflection coefficient

As is the case with the h and y matrices, the suffixes e and b denote the common-emitter and common-base configurations respectively.

	[h]		[y]		[5	5]
[1.]	h <sub>i</sub>	h <sub>r</sub>	$\frac{1}{y_i}$	$-\frac{y_r}{y_i}$	$(1 + s_i)(1 + s_i$	$\frac{s_0) - s_r s_f}{s_0) + s_r s_f}$ $\frac{2s_r}{1 + s_0) + s_r s_f}$
[h]	h <sub>f</sub>	h <sub>o</sub>	Y <sub>f</sub> Y <sub>i</sub>	y <sub>i</sub> y <sub>o</sub> - y <sub>r</sub> y <sub>f</sub> y <sub>i</sub>	$\begin{array}{c} -2s_{f} \\ \hline (1-s_{i})(1+s_{i}) \\ (1-s_{i})(1-s_{i})(1-s_{i})(1-s_{i})(1-s_{i})(1-s_{i}) \end{array}$	$(s_0) + s_r s_f$ $(1 - s_0) - s_r s_f$ $(1 + s_0) + s_r s_f$
[y]	1 h <sub>i</sub>	- hr hi	Уi	Уr	$\frac{(1 - s_i)(1 + s_i)(1 + s_i)(1 + s_i)(1 + s_i)}{(1 + s_i)(1 + s_i)(1 + s_i)(1 + s_i)(1 + s_i)(1 + s_i)}$	$\frac{s_{0} + s_{r} + s_{f}}{s_{0} - s_{r} + s_{f}}$ $\frac{-2s_{r}}{1 + s_{0} - s_{r} + s_{f}}$
ΓλΊ	h <sub>f</sub> h <sub>i</sub>	<u>hi</u> ho - hr h <sub>f</sub> hi	Уf	Уо	$\begin{array}{c} -2s_{f} \\ \hline (1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1+s_{i})(1$	$(s_0) - s_r s_f$ $(1 - s_0) + s_r s_f$ $(1 + s_0) - s_r s_f$
	$\frac{(h_{i} - 1)(h_{0} + 1) - h_{r} h_{f}}{(h_{i} + 1)(h_{0} + 1) - h_{r} h_{f}}$ $\frac{2h_{r}}{(h_{i} + 1)(h_{0} + 1) - h_{r} h_{f}}$		$\frac{(1 - y_{i})(1 + y_{o}) + y_{r}y_{f}}{(1 + y_{i})(1 + y_{o}) - y_{r}y_{f}}$ $\frac{-2y_{r}}{(1 + y_{i})(1 + y_{o}) - y_{r}y_{f}}$		Sį	Sr
[s]		$\frac{f}{f} + 1) - h_r h_f + h_r h_r + h_r + h_r h_r + h_r$		0, 111	Sf	S <sub>O</sub>

#### Table 1.3 Interrelation of parameters

		Converted h parameters					
		Commo	on-base	Common-	emitter	Common-collector	
	Common-base			$\frac{h_{ib}}{1 + h_{fb}}$	$\frac{\Delta h_b - h_{rb}}{1 + h_{fb}}$	$\frac{h_{ib}}{1 + h_{fb}}$	1
	Commo			$\frac{-h_{fb}}{1+h_{fb}}$	h <sub>ob</sub> 1 + h <sub>fb</sub>	$\frac{-1}{1 + h_{fb}}$	$\frac{h_{ob}}{1 + h_{fb}}$
Known h parameters	Common-emitter	$\frac{h_{ie}}{1 + h_{fe}}$	$\frac{\Delta h_e - h_{re}}{1 + h_{fe}}$			h <sub>ie</sub>	1 - h <sub>re</sub>
Known h p	Commor	$-h_{fe}$ 1 + $h_{fe}$	$\frac{h_{oe}}{1 + h_{fe}}$			-(1+ $h_{fe}$ )	h <sub>oe</sub>
	Common-collector	-h <sub>ic</sub> h <sub>fc</sub>	<u>-Δh<sub>rc</sub></u> - 1 h <sub>fc</sub> - 1	h <sub>ic</sub>	1 - h <sub>rc</sub>		
	Commor	$\frac{-(1 + h_{fc})}{h_{fc}}$	- h <sub>oc</sub> h <sub>fc</sub>	-(1+h <sub>fc</sub> )	h <sub>oc</sub>		

#### Table 1.4 Conversion formulas for h parameters

 $\Delta h_e = \ h_{ie} \ h_{oe} - \ h_{re} \ h_{fe} \ , \ \ \Delta h_b = \ h_{ib} \ h_{ob} - \ h_{rb} \ h_{fb} \ , \ \ \Delta h_c = \ h_{ic} \ h_{oc} - \ h_{rc} \ h_{fc}$ 

		Converted y parameters				
		Common-base	Common-emitter	Common-collector		
	Common-base		$\sum y_b \qquad -(y_{rb} + y_{ob})$	$\sum y_b \qquad -(y_{ib} + y_{fb})$		
ers	Commo		$-(y_{fb} + y_{ob}) y_{ob}$	-( $y_{ib} + y_{rb}$ ) $y_{ib}$		
Known y parameters	Common-emit ter	$\sum y_e$ -( $y_{re} + y_{oe}$ )		$y_{ie}$ -( $y_{ie} + y_{re}$ )		
у пооп	Comme	-( $y_{fe} + y_{oe}$ ) $y_{oe}$		-( $y_{ie} + y_{fe}$ ) $\sum y_e$		
	Common-colle ctor	$y_{oc}$ -( $y_{fc} + y_{oc}$ )	$y_{ic}$ -( $y_{ic} + y_{rc}$ )			
	Comme	-( $y_{rc} + y_{oc}$ ) $\sum y_c$	-( $y_{ic} + y_{fc}$ ) $\sum y_{c}$			

#### Table 1.5 Conversion formulas for y parameters

 $\Sigma y_e = y_{ie} + y_{re} + y_{fe} + y_{oe}$ 

 $\Sigma y_b = y_{ib} + y_{rb} + y_{fb} + y_{ob}$ 

 $\Sigma y_{\rm C} = y_{\rm iC} + y_{\rm rC} + y_{\rm fC} + y_{\rm oC}$ 

	Common-base		Common-emitter
h <sub>ib</sub>	$\frac{r_{e} + r_{bb'} \left[ (1 - \alpha_{0}) + j \frac{f}{f_{\alpha}} \right]}{1 + j \frac{f}{f_{\alpha}}}$	h <sub>ie</sub>	$r_{bb'} + \frac{r_e}{(1 - \alpha_0) + j \frac{f}{f_\alpha}}$
h <sub>rb</sub>	j2πfC <sub>c</sub> r <sub>bb'</sub>	h <sub>re</sub>	$2\pi f_{\alpha} C_{c} r_{e} \frac{j \frac{f}{f_{\alpha}}}{(1 - \alpha_{0}) + j \frac{f}{f_{\alpha}}}$
h <sub>fb</sub>	$\frac{-\alpha_0}{1+j\frac{f}{f_\alpha}}$	h <sub>fe</sub>	$\frac{\alpha_0}{(1 - \alpha_0) + j \frac{f}{f_\alpha}}$
h <sub>ob</sub>	j2πfC <sub>c</sub>	h <sub>oe</sub>	$2 \pi f_{\alpha} C_{c} \frac{j \frac{f}{f_{\alpha}} \left(1 + j \frac{f}{f_{\alpha}}\right)}{(1 - \alpha_{0}) + j \frac{f}{f_{\alpha}}}$

 Table 1.6 h parameters converted using T-type equivalent circuit

#### Table 1.7 y parameters converted using T-type equivalent circuit

	Common-base		Common-emitter
Уіb	$\frac{1 + j \frac{f}{f_{\alpha}}}{r_{e} + j r_{bb'} \frac{f}{f_{\alpha}}}$	Yie	$\frac{(1 - \alpha_0) + j \frac{f}{f_{\alpha}}}{r_e + j r_{bb'} \frac{f}{f_{\alpha}}}$
Угь	$-2\pi f_{\alpha} C_{c} \frac{j - \frac{f}{f_{\alpha}} \left(1 + j - \frac{f}{f_{\alpha}}\right)}{\frac{r_{e}}{r_{bb'}} + j - \frac{f}{f_{\alpha}}}$	Уге	$-2\pi f_{\alpha}C_{c} \frac{r_{e}}{r_{bb'}} \frac{j\frac{f}{f_{\alpha}}}{\frac{r_{e}}{r_{bb'}} + j\frac{f}{f_{\alpha}}}$
Уfb	$\frac{\alpha_0}{r_e + j r_{bb'} \frac{f}{f_{\alpha}}}$	Уfe	$\frac{\alpha_0}{r_e + j r_{bb'} \frac{f}{f_{\alpha}}}$
Уор	$2\pi f_{\alpha}C_{c} \frac{j\frac{f}{f_{\alpha}}\left(1+\frac{r_{e}}{r_{bb'}}+j\frac{f}{f_{\alpha}}\right)}{\frac{r_{e}}{r_{bb'}}+j\frac{f}{f_{\alpha}}}$	Уое	Same as for y <sub>ob</sub>

#### Bipolar Transistors Application Note



See Table 1.3 to Table 1.5 for the relationships among the circuit parameters and the conversion between the common-base and common-emitter parameters. Figure 1.7 and Figure 1.8 show the frequency loci of the h and y parameters obtained from Table 1.6 and Table 1.7 respectively. The parameters described above vary with the operating point and temperature. Circuit designers should understand their effects on the parameters.

#### 1.3. Low-frequency, low-noise amplifiers

(1) Designing low-noise amplifiers

It is necessary to select and use transistors carefully when designing low-noise amplifiers. Voltage, current, and signal source impedance should be considered to ensure that the transistors are used within the ranges that exhibit the best performance of the transistors. To help circuit designers obtain the best performance from low-noise transistors, this section describes the concept of noise characteristics, the optimal conditions of transistors, and the relationships between the noise figures of transistors and the S/N ratios of amplifiers.

#### (2) Noise characteristics of transistors

The noise figure (NF) of a transistor is given by:

- E<sub>si</sub> : Input signal voltage
- E<sub>ni</sub> : Input noise voltage
- E<sub>so</sub> : Output signal voltage
- Eno : Output noise voltage
- k : Boltzmann constant (1.38×10<sup>-23</sup> J/ °K)
- T : Absolute temperature (K)
- R<sub>g</sub> : Signal source resistance
- B : Noise bandwidth (Hz)

or 
$$E_{ni} = \sqrt{4 \, k \, T \, R_g \, B}$$

Figure 1.9 shows the NF-vs-frequency curve, which is divided into three regions: 1) 1/ f region, 2) white noise region, and 3)  $f^2$  noise region.



Figure 1.9 Relationship between NF and frequency

Type Item	1/ f noise region	White noise region	f <sup>2</sup> noise region
Description	Noise decreases at -3 dB/ oct in proportion to frequency f.	Noise remains constant	Noise increases at 6 dB/ oct in proportion to frequency f.
Cause	Surface fluctuation	the base spreading	Fluctuation caused by current separation
Audio applications	Noise generated	Noise generated	Not noise generated

Table 1.8 Types of noise

A transistor can be modeled with a voltage noise source  $(e_N)$  and a current noise source

 $(i_N)$  as shown below.



$$e_{N} = \sqrt{4 \text{ k T R}_{N} \text{ B}}$$
$$i_{N} = \sqrt{2 \text{ q I}_{b} \text{ B}}$$

 $R_N$ : Equivalent noise resistance ( $\Omega$ )

q : Elementary charge  $1.602 \times 10^{-19}$  (C)

#### Figure 1.10 Noise source of transistor

Considering the ideal transistor without any noise source, the noise figure (NF) is given by:  $NF = 10 \log I$ 

B : 1Hz

 $\gamma$   $\ : \ Correlation function of <math display="inline">e_N$  and  $i_N$ 

Equation 1-13 shows that NF is a function of  $e_N$  and  $i_N$ .

It is evident from Equation 1-13 that the noise figure NF is dependent on the collector

current  $I_C$  and the signal source impedance  $R_g$ . Let the total noise voltage be  $e_{NT}$ . Then,

$$\overline{e}_{NT}^2 = 4 \text{ k T } R_g + e_N^2 + i_N^2 R_g^2 + 2 \gamma e_N i_N$$
 (1-14)

Figure 1.11 shows the relationship between the total noise voltage and the signal source impedance  $R_{\rm q}.$ 



Figure 1.11 Total noise voltage – Signal source resistance

Referring to the curve of Device C in Figure 1.11, the noise figure can be seen as a difference (B) between its noise voltage and the thermal noise at  $R_g = 100 \Omega$ .

NF = 20 (  $\log \beta - \log \alpha$  )  $\rightarrow$  B in Figure 1.11

As can be seen from Equation 1-14, voltage noise is more dominant in the small  $R_g$  region. However, current noise is dominant in the region where Rg increases.

 $R_g$ ,  $I_C$ , and noise figure can be shown by plotting contours of the constant noise figure as shown in Figure 1.12 and Figure 1.13.



Figure 1.12 NF –  $R_g$ ,  $I_C(1)$ 



These noise figure contours can be used to determine the optimal usage condition of an amplifier.

Use the signal source impedance of the amplifier to obtain the collector current  $I_C$  at which the noise figure is minimum from the noise figure contours at f = 1 kHz and f = 10 Hz. When designing a low-noise amplifier, it is necessary to consider the conditions of the circuits preceding and following the amplifier. The next subsection describes an amplifier's noise, considering the foregoing.

#### (3) Amplifier noise

The signal-to-noise (SN) ratio is an important factor in designing an amplifier.

 $SN = 20 \log \frac{Rate output}{Output noise voltage}$  (dB) (1-15)

From Equation 1-12, Equation 1-15 can be restated as follows to include NF.

$$SN = 20 \log \frac{E_{SO}}{E_{nO}}$$

$$= 10 \log \frac{E_{SO}^{2}}{E_{nO}^{2}}$$

$$= 10 \log \left( \frac{E_{Si}^{2}}{E_{nO}^{2}} \cdot 10^{\frac{NF}{10}} \right)$$

$$= 10 \log \frac{E_{Si}^{2}}{4 \text{ k T Rg B}} - \text{NF} (\text{ dB}) \quad \dots \quad (1-16)$$

Amplifier's S/ N ratio	_	Input S/ N ratio (dB)	_	Amplifier's NF (dB)
(dB)	_			

Noise figure of multi-stage amplifiers

The noise figure of a multi-stage amplifier like the one shown in Figure 1.14 can be calculated as follows:

$$NF_{T} = NF_{1} + \frac{NF_{2} - 1}{G_{1}} + \frac{NF_{3} - 1}{G_{1} G_{2}}$$
(1-17)





The equivalent noise resistance  $(R_N)$  of this amplifier is:



Figure 1.15 Equivalent noise resistance of a multi-stage amplifier

Equation 1-17 and Equation 1-18 indicate that, if the power gain of the first amplifier  $(A_1)$  is sufficiently large, the total noise figure NF<sub>T</sub> is:

 $NF_T \approx NF_1$  (1-19)

The total noise figure of the multi-stage amplifier is close to that of the first amplifier.

# Calculating the total noise figure $NF_T$ of a multi-stage amplifier from the nominal NF parameters of transistors

The NF values in the transistor datasheets are the measurements taken at spot frequencies (such as 1 kHz, 100 Hz, and 10 Hz). These values cannot be used without adjustment to design a wide-bandwidth amplifier with low-frequency boost. Since the  $f^2$  noise region lies in the high-frequency region, only the 1/ f and white noise regions are related to low-frequency amplification.

Assuming:

$\left[ \overline{e_g}^2 \right]$	2	: Mean square voltage of the thermal noise	
		generated by signal source resistance $R_g$	(1–20)
$\overline{e}_w$	2	Mean square voltage of white noise	
e⁻	<sup>2</sup> 1/f	Mean square voltage of 1/ f noise	

the following equation is derived from the definition of the noise figure:

$$\frac{NF \text{ (white noise region)} =}{\frac{\overline{e_g}^2 + \overline{e_w}^2}{\overline{e_g}^2}} = NF_{(1kHz)}$$
(1-21)

 $NF_{(1kHz)}$  : NF at the 1-kHz spot frequency

 $\overline{e}_{w}^{2}$  is calculated as follows from Equation 1-20:

$$\overline{e}_{W}^{2} = (NF_{(1kHz)} - 1)\overline{e}_{g}^{2}$$
 (1-22)

Let the noise figure at 10 Hz be  $NF_{(10Hz)}$ . Then,

From Equation (1-22),

$$\overline{e}_{g^{2}}^{2} (I_{10 \text{ Hz}}) = (NF_{(10 \text{ Hz})} - NF_{(1 \text{ kHz})})$$

$$\overline{e}_{g^{2}}^{2} (1-24)$$

Since the 1/ f noise decreases at -3 dB/ oct in proportion to frequency,  $\overline{e}_{1/f}^2$  at a normal frequency can be calculated as follows:

$$\overline{e}_{1/f}^{2} = (NF_{(10 \text{ Hz})} - NF_{(1 \text{ kHz})}) \overline{e}_{g^{2}} \frac{10}{f} \dots (1-25)$$

References

1) WILLIAM A.RHEINFELDER : DESIGN OF LOW NOISE TRANSISTOR INPUT CIRCUITS, LONDON ILIFFE BOOKS LTD. (1964)

2 )J.WATSON : SEMICONDUCTOR CIRCUIT DESIGN, ADAM HILGE LTD. (1970)

#### **RESTRICTIONS ON PRODUCT USE**

Toshiba Corporation and its subsidiaries and affiliates are collectively referred to as "TOSHIBA". Hardware, software and systems described in this document are collectively referred to as "Product".

- TOSHIBA reserves the right to make changes to the information in this document and related Product without notice.
- This document and any information herein may not be reproduced without prior written permission from TOSHIBA. Even with TOSHIBA's written permission, reproduction is permissible only if reproduction is without alteration/omission.
- Though TOSHIBA works continually to improve Product's quality and reliability, Product can malfunction or fail. Customers are responsible for complying with safety standards and for providing adequate designs and safeguards for their hardware, software and systems which minimize risk and avoid situations in which a malfunction or failure of Product could cause loss of human life, bodily injury or damage to property, including data loss or corruption. Before customers use the Product, create designs including the Product, or incorporate the Product into their own applications, customers must also refer to and comply with (a) the latest versions of all relevant TOSHIBA information, including without limitation, this document, the specifications, the data sheets and application notes for Product and the precautions and conditions set forth in the "TOSHIBA Semiconductor Reliability Handbook" and (b) the instructions for the application with which the Product will be used with or for. Customers are solely responsible for all aspects of their own product design or applications, including but not limited to (a) determining the appropriateness of the use of this Product in such design or applications; (b) evaluating and determining the applicability of any information contained in this document, or in charts, diagrams, programs, algorithms, sample application circuits, or any other referenced documents; and (c) validating all operating parameters for such designs and applications.
- PRODUCT IS NEITHER INTENDED NOR WARRANTED FOR USE IN EQUIPMENTS OR SYSTEMS THAT REQUIRE EXTRAORDINARILY HIGH LEVELS OF QUALITY AND/OR RELIABILITY, AND/OR A MALFUNCTION OR FAILURE OF WHICH MAY CAUSE LOSS OF HUMAN LIFE, BODILY INJURY, SERIOUS PROPERTY DAMAGE AND/OR SERIOUS PUBLIC IMPACT ("UNINTENDED USE"). Except for specific applications as expressly stated in this document, Unintended Use includes, without limitation, equipment used in nuclear facilities, equipment used in the aerospace industry, lifesaving and/or life supporting medical equipment, equipment used for automobiles, trains, ships and other transportation, traffic signaling equipment, equipment used to control combustions or explosions, safety devices, elevators and escalators, and devices related to power plant. IF YOU USE PRODUCT FOR UNINTENDED USE, TOSHIBA ASSUMES NO LIABILITY FOR PRODUCT. For details, please contact your TOSHIBA sales representative or contact us via our website.
- Do not disassemble, analyze, reverse-engineer, alter, modify, translate or copy Product, whether in whole or in part.
- Product shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable laws or regulations.
- The information contained herein is presented only as guidance for Product use. No responsibility is assumed by TOSHIBA for any infringement of patents or any other intellectual property rights of third parties that may result from the use of Product. No license to any intellectual property right is granted by this document, whether express or implied, by estoppel or otherwise.
- ABSENT A WRITTEN SIGNED AGREEMENT, EXCEPT AS PROVIDED IN THE RELEVANT TERMS AND CONDITIONS OF SALE FOR PRODUCT, AND TO THE MAXIMUM EXTENT ALLOWABLE BY LAW, TOSHIBA (1) ASSUMES NO LIABILITY WHATSOEVER, INCLUDING WITHOUT LIMITATION, INDIRECT, CONSEQUENTIAL, SPECIAL, OR INCIDENTAL DAMAGES OR LOSS, INCLUDING WITHOUT LIMITATION, LOSS OF PROFITS, LOSS OF OPPORTUNITIES, BUSINESS INTERRUPTION AND LOSS OF DATA, AND (2) DISCLAIMS ANY AND ALL EXPRESS OR IMPLIED WARRANTIES AND CONDITIONS RELATED TO SALE, USE OF PRODUCT, OR INFORMATION, INCLUDING WARRANTIES OR CONDITIONS OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, ACCURACY OF INFORMATION, OR NONINFRINGEMENT.
- Do not use or otherwise make available Product or related software or technology for any military purposes, including without limitation, for the design, development, use, stockpiling or manufacturing of nuclear, chemical, or biological weapons or missile technology products (mass destruction weapons). Product and related software and technology may be controlled under the applicable export laws and regulations including, without limitation, the Japanese Foreign Exchange and Foreign Trade Law and the U.S. Export Administration Regulations. Export and re-export of Product or related software or technology are strictly prohibited except in compliance with all applicable export laws and regulations.
- Please contact your TOSHIBA sales representative for details as to environmental matters such as the RoHS compatibility of Product. Please use Product in compliance with all applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive. TOSHIBA ASSUMES NO LIABILITY FOR DAMAGES OR LOSSES OCCURRING AS A RESULT OF NONCOMPLIANCE WITH APPLICABLE LAWS AND REGULATIONS.

## **Toshiba Electronic Devices & Storage Corporation**

https://toshiba.semicon-storage.com/