

Comparison of SiC MOSFET and Si IGBT

Description

This document explains the comparison of Toshiba SiC MOSFET TW070J120B and Si IGBT, by switching loss, conduction loss, diode loss, and total power loss simulation.

Table of Contents

Description.....	1
Table of Contents.....	2
1. SiC Power Devices	4
2. SiC MOSFET Features	5
3. Power Loss Comparison of SiC MOSFET and Si IGBT.....	5
3.1 Rg-dependency of Turn-on and Turn-off Switching Loss ^(Note 1)	5
3.2 Turn-on Switching Waveforms and Turn-on Switching Loss ^(Note2)	6
3.3 Turn-off Switching Waveform and Turn-off Switching Loss ^(Note3)	7
3.4 On-resistance Characteristics	8
3.5 Diode Forward Voltage Characteristic.....	9
4. Power Loss Simulation.....	9
RESTRICTIONS ON PRODUCT USE	10

List of Figures

Figure 1-1 Structure of a Double-diffused MOSFET	5
Figure 3-1 SiC MOSFET and Si IGBT, R_g -dependency of turn-on switching loss.....	6
Figure 3-2 SiC MOSFET and Si IGBT, R_g -dependency of turn-off switching loss.....	6
Figure 3-3 Turn-on Switching Waveform of SiC MOSFET and Si IGBT	6
Figure 3-4 Turn-on Switching Loss of SiC MOSFET and Si IGBT	7
Figure 3-5 Turn-off Waveform of SiC MOSFET and Si IGBT	7
Figure 3-6 Turn-off Switching Loss of SiC MOSFET and Si IGBT	8
Figure 3-7 $I_D - V_{DS}$ Curve of SiC MOSFET and $I_C - V_{CE}$ Curve of Si IGBT	8
Figure 3-8 $I_F - V_F$ Curves of SiC MOSFET and Si IGBT	9
Figure 4-1 Power Loss Simulation Results	9

Table of Contents

Table 1-1 Physical Properties of Typical Semiconductor Materials	4
Table 1-2 Simulated on-resistances of a double-diffused Si MOSFET	5

1. SiC Power Devices

Silicon carbide (SiC) comprises silicon (Si) and carbon (C) atoms. Each atom is surrounded by four different atoms in the form of a regular tetrahedron. SiC is a compound semiconductor with the densest tetrahedral arrangement. SiC has many crystalline structures called polytypes that exhibit different physical properties because of periodic differences in the overlap of tetrahedrons.

Compared to silicon, SiC has a wider energy gap where no electron states can exist (called a bandgap) between the valence band (i.e., an energy band filled with valence electrons) and the conduction band (i.e., an empty energy band in which electrons can be present). A wide bandgap provides a strong chemical bond among atoms and therefore a high electric breakdown field. SiC has an electric breakdown field roughly ten times that of silicon. Because of a strong atomic bond, SiC has greater lattice vibration and consequently conducts energy more easily than silicon. Therefore, SiC is a semiconductor material with good thermal conduction. The polytypes of SiC include 4H-SiC and 6H-SiC that are hexagonal crystal structures and 3C-SiC that is a cubic crystal structure. Table 1-1 compares the physical properties of silicon and other semiconductor materials. 4H-SiC is commonly used as a semiconductor material because it provides a better balance among electron mobility, dielectric breakdown strength, saturation velocity, and other physical properties than other polytypes of SiC.

Table 1-1 Physical Properties of Typical Semiconductor Materials

Property	Unit	Si	4H-SiC	6H-SiC	3C-SiC	GaN	GaAs	Diamond
Bandgap	eV	1.12	3.26	3.02	2.23	3.39	1.43	5.47
Electron mobility μ_e	cm ² /Vs	1400	1000 ⊥ to c-axis	450 ⊥ to c-axis	1000	900	8500	2200
Hole mobility μ_h			1200 to c-axis	100 to c-axis				
Electric breakdown field E_c	V/cm	3.0×10^5	2.8×10^6	3.0×10^6	1.5×10^6	3.3×10^6	4.0×10^5	1.0×10^7
Thermal conductivity λ	W/cmK	1.5	4.9	4.9	4.9	2.0	0.5	20
Saturated electron drift velocity V_{sat}	cm/s	1.0×10^7	2.2×10^7	1.9×10^7	2.7×10^7	2.7×10^7	2.0×10^7	2.7×10^7
Relative dielectric constant ϵ		11.8	9.7 ⊥ to c-axis 10.2 to c-axis	9.7 ⊥ to c-axis 10.2 to c-axis	9.7	9.0	12.8	5.5

As shown in Table 1-2, the resistance of the drift region accounts for a large percentage of the on-resistance per area of high-voltage power devices. To reduce on-resistance, it is necessary to either increase the dopant concentration in the drift region or reduce its thickness. However, the dopant concentration is inversely proportional to the withstand voltage. In the case of silicon with low breakdown strength, it is impossible to further increase the dopant concentration without compromising the withstand voltage. It is also difficult to reduce the thickness of the drift region of a silicon device because the expansion of the depletion region could cause punch-through (between drain and source) when a reverse bias is applied across the drain and source. SiC power devices with breakthrough performance have been appearing lately because the dielectric breakdown strength of 4H-SiC is nearly ten times that of silicon as shown in Table 1-1. For example, the withstand voltage of a MOSFET can be simply expressed as:

$$\text{Withstand voltage} = \text{maximum electric breakdown field} \times \text{depletion region thickness} \div 2$$

(The assumption is a triangular electric field distribution.)

This equation indicates that because of a higher electric breakdown field than that of silicon, SiC makes it possible to increase the dopant concentration in the drift region and thereby reduce its thickness to obtain the same withstand voltage. Electron and hole mobilities (μ) characterize how quickly an electric field can accelerate the velocity of an electron or a hole (velocity = mobility (μ) \times electric field (E)). A higher mobility (μ) means that an electric current flows more easily, resulting in lower resistance. The maximum velocity attainable is called the saturation velocity.

Table 1-2 Simulated on-resistances of a double-diffused Si MOSFET

Withstand Voltage	600V	1000V
R_{ch}	1%	0.3%
R_{JFET}	18%	14%
R_{drift}	81%	86%
R_{sub}	0.1%	0.03%
TTL	100%	100%

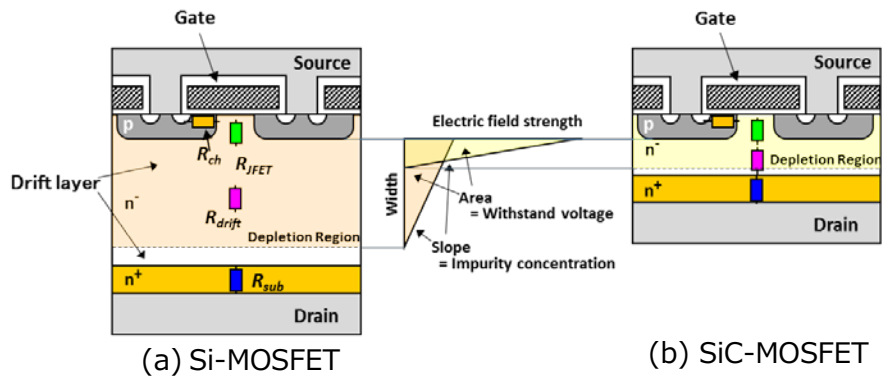


Figure 1-1 Structure of a double-diffused MOSFET

In addition, the high thermal conductivity (λ) of SiC makes it ideal as a material for high-power semiconductor devices.

SiC makes it possible to create high-voltage power devices with unprecedentedly low on-resistance thanks to a heavily doped thin drift region as shown in Figure 1-1 (b).

2. SiC MOSFET Features

Since the dielectric breakdown strength of SiC is about 10 times as high as that of Si, a power device with high withstand voltage and low voltage drop can be realized. In the case of the same withstand voltage, the on-resistance per unit area can be reduced compared with that of Si. In addition, while Si MOSFET is generally commercialized only up to about 1000V, SiC MOSFET is commercialized up to about 3300V because it can keep on-resistance low even at high withstand voltages. IGBT, the bipolar device, is commonly used as Si high-voltage transistors of 1000V or higher. IGBT have bipolar operation with two types of carriers, electron and hole, by injecting minority carriers, holes, into the drift layer, thereby lowering the resistance in the drift layer. However, the disadvantage of bipolar operation is that the tail current generated at turn-off due to the accumulation of minority carriers, which make increase turn-off loss.

On the other hand, SiC can realize MOSFET, the unipolar device that operates only with electrons even in high-voltage products, and the turn-off loss is smaller than bipolar devices because no tail current is generated. For this reason, SiC MOSFET is attracting attention because it can operate in the high switching frequency, which was difficult for Si IGBT, and it also contributes to the miniaturization of passive components.

This report makes comparison for the switching loss, conduction loss, and diode loss of SiC MOSFET and Si IGBT, and introduces examples of power loss simulation.

3. Power Loss Comparison of SiC MOSFET and Si IGBT

3.1 Rg-dependency of Turn-on and Turn-off Switching Loss (Note 1)

For both turn-on and turn-off switching loss, SiC MOSFET (TW070J120B) can reduce them compared to Si IGBT (Company A: High Speed Switching type).

(Note 1) IGBT test conditions:

$V_{CC}=800\text{ V}$, $I_C=10\text{ A}$, $T_a=25\text{ }^\circ\text{C}$, $150\text{ }^\circ\text{C}$, $V_{GE} = 20\text{ V} / -5\text{ V}$, Inductive Load: $L = 1\text{ mH}$,

IGBT emitter-to-collector diode is used as freewheeling diode (FWDs) in parallel with inductive load.

SiC MOSFET test conditions:

$V_{DD} = 800\text{ V}$, $I_D = 10\text{ A}$, $T_a = 25\text{ }^\circ\text{C}$, $150\text{ }^\circ\text{C}$, $V_{GS} = 20\text{ V} / -5\text{ V}$, Inductive Load: $L = 1\text{ mH}$,

TW070J120B source-drain diode is used as freewheeling diode (FWDs) in parallel with inductive load.

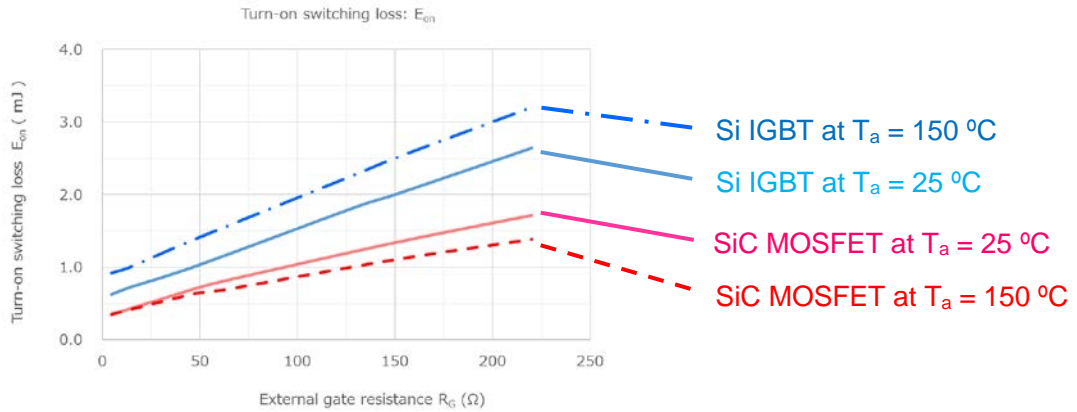


Figure 3-1 SiC MOSFET and Si IGBT, R_G -dependency of turn-on switching loss

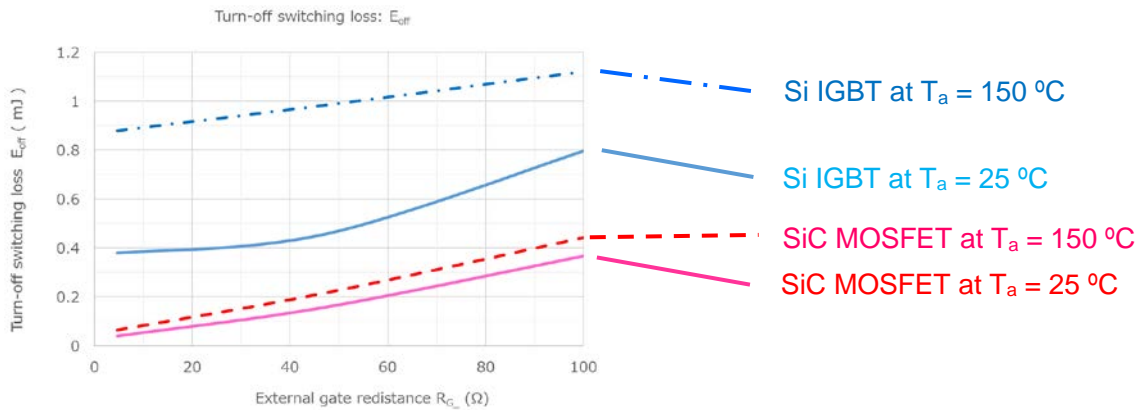


Figure 3-2 SiC MOSFET and Si IGBT, R_G -dependency of turn-off switching loss

3.2 Turn-on Switching Waveforms and Turn-on Switching Loss (Note2)

(Note 2)

IGBT test condition: external gate resistance $R_G = 150\text{ }\Omega$, others are the same test condition as (Note 1).

SiC MOSFET test condition: external gate resistance $R_G = 47\text{ }\Omega$; others are the same test condition as (Note 1).

In order to equalize current slope at turn-on, the test conditions is set as above.

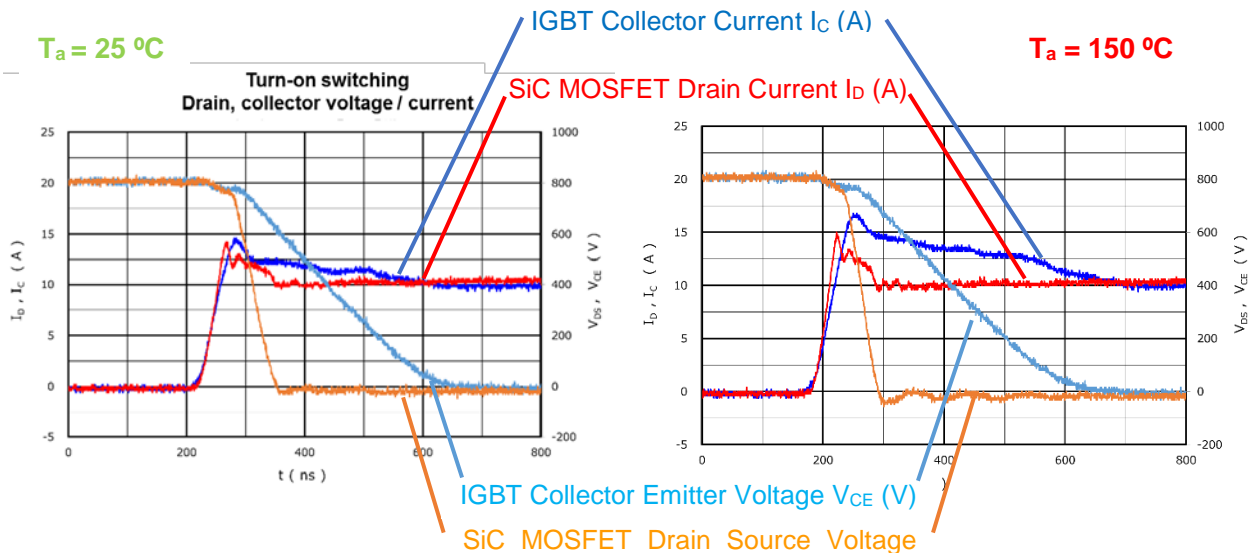


Figure 3-3 Turn-on Switching Waveform of SiC MOSFET and Si IGBT



Figure 3-4 Turn-on Switching Loss of SiC MOSFET and Si IGBT

Turn-on switching-loss E_{on}	$T_a = 25\text{ }^\circ\text{C}$	$T_a = 150\text{ }^\circ\text{C}$
E_{on} of IGBT (mJ)	2.0	2.5
E_{on} of SiC MOSFET (mJ)	0.7	0.6
From IGBT to SiC MOSFET E_{on} reduction rate	65% reduced	76% reduced

3.3 Turn-off Switching Waveform and Turn-off Switching Loss (Note3)

(Note 3) IGBT, SiC MOSFET test conditions:

The external gate resistor R_G is 47 Ω . Otherwise, the test conditions are the same as (Note 1).

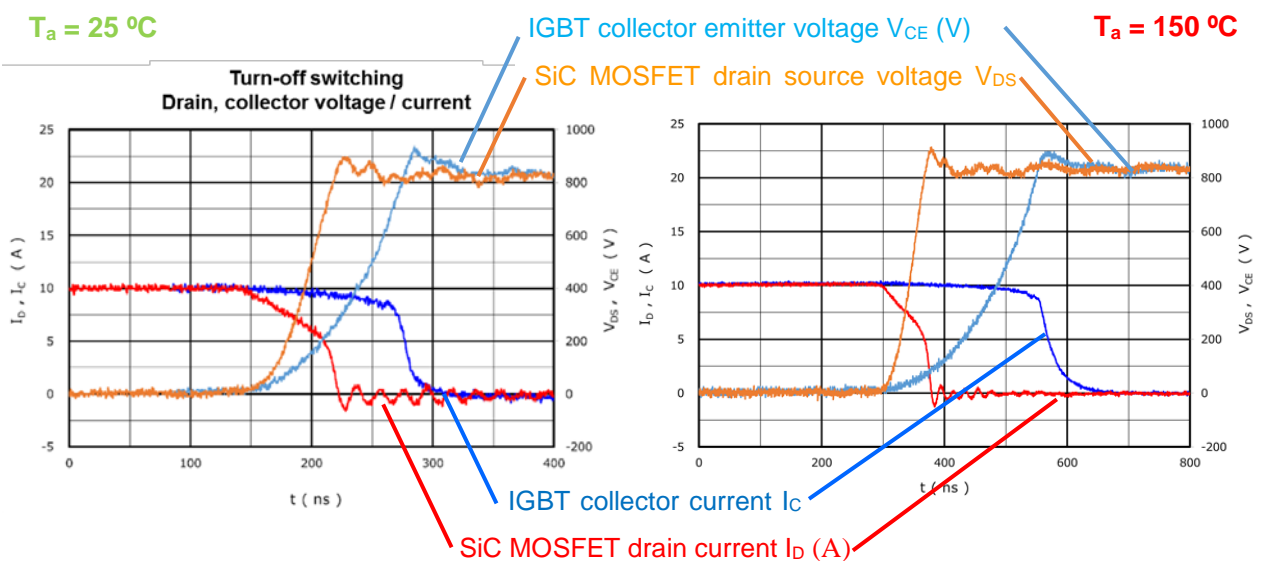


Figure 3-5 Turn-off Waveform of SiC MOSFET and Si IGBT



Figure 3-6 Turn-off Switching Loss of SiC MOSFET and Si IGBT

Turn-off switching-loss E_{off}	$T_a = 25\text{ }^\circ\text{C}$	$T_a = 150\text{ }^\circ\text{C}$
E_{off} of IGBT (mJ)	0.46	0.98
E_{off} of SiC MOSFET (mJ)	0.16	0.22
From IGBT to SiC MOSFET E_{off} reduction rate	65% reduced	77% reduced

3.4 On-resistance Characteristics

SiC MOSFET (TW070J120B) can reduce the on-voltage characteristic $V_{DS(on)}$ ($V_{CE(sat)}$) in the area below $T_a = 150\text{ }^\circ\text{C}$, I_D (I_C) = 25A compared to Si IGBT (Company A: High Speed Switching type).

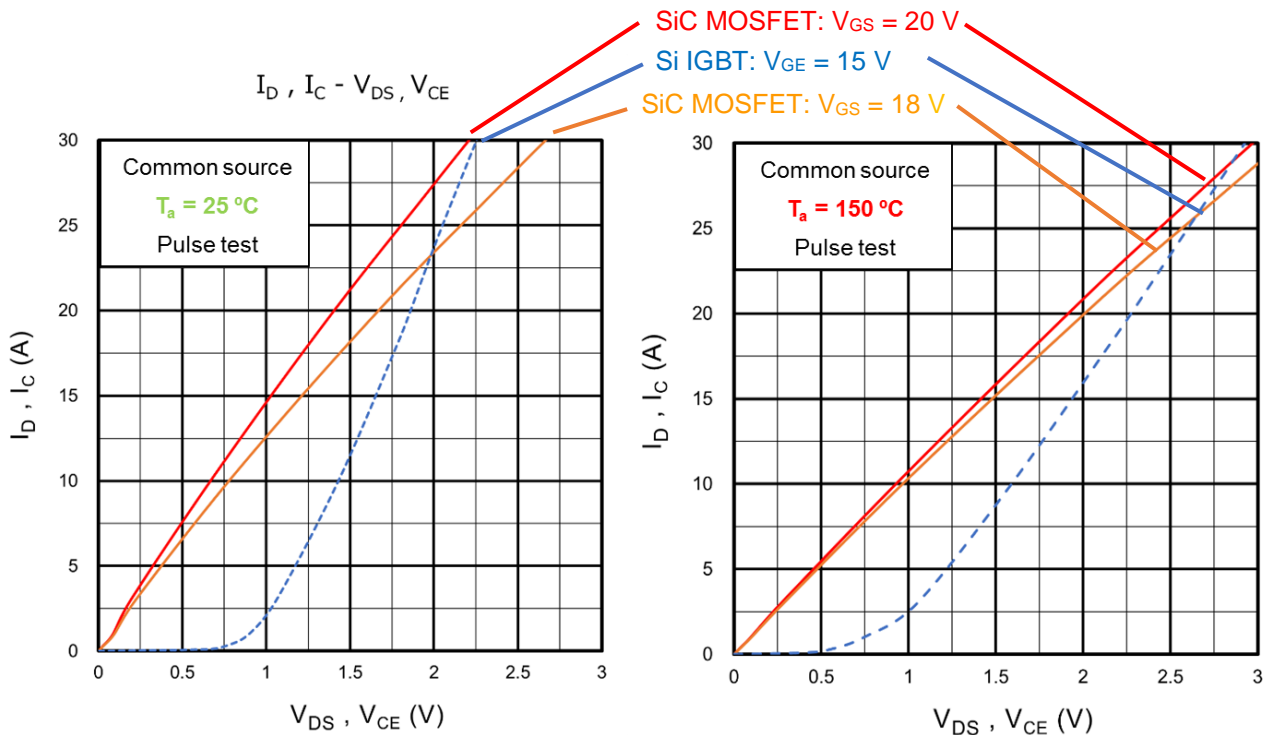


Figure 3-7 $I_D - V_{DS}$ Curve of SiC MOSFET and $I_C - V_{CE}$ Curve of Si IGBT

3.5 Diode Forward Voltage Characteristic

SiC MOSFET (TW070J120B) has a lower diode-forward voltage V_F than Si IGBT (Company A: High Speed Switching type) when $T_a = 25\text{ }^\circ\text{C}$, $I_F = 0.8\text{ A}$ or higher, and is comparable when $T_a = 150\text{ }^\circ\text{C}$, $I_F = 3\text{ A}$ or higher.

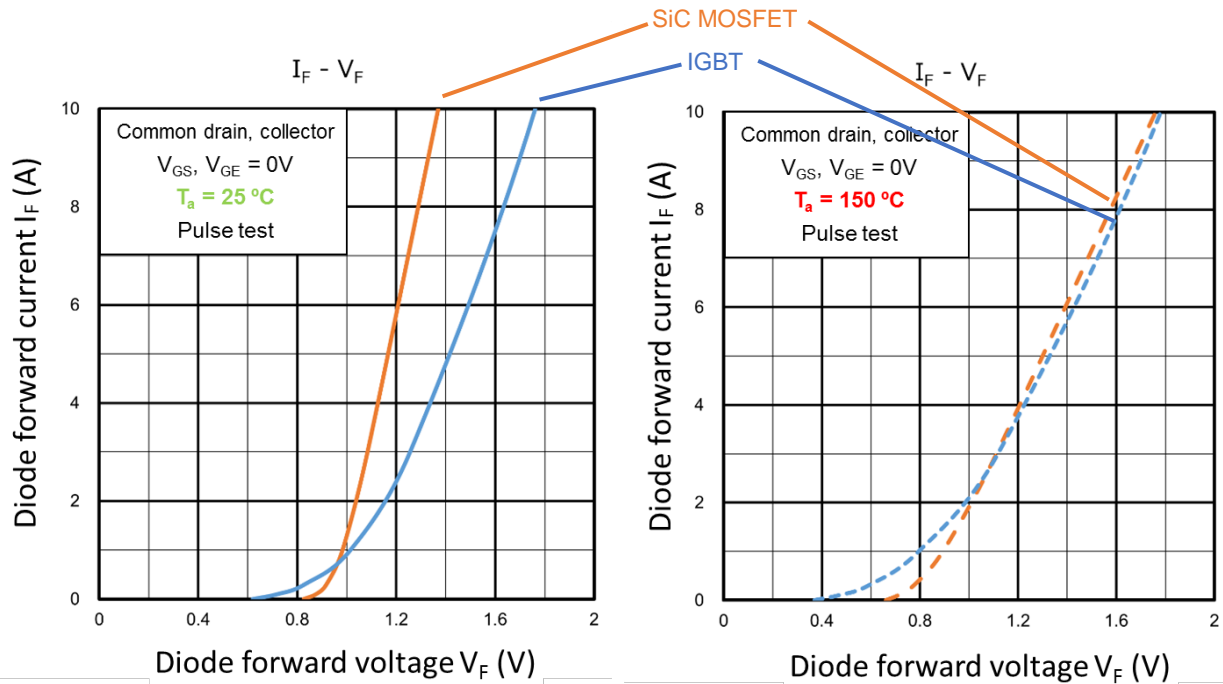


Figure 3-8 $I_F - V_F$ Curves of SiC MOSFET and Si IGBT

4. Power Loss Simulation

Using the switching characteristics, on-resistance characteristics, and diode-forward voltage characteristics of SiC MOSFET (TW070J120B) and Si IGBT, Power Loss is simulated with conditions as $V_{cc} = 400V$, $I_o = 7.0\text{ Arms}$, P.F. = 1, three-phase modulation, and $T_j = 150\text{ }^\circ\text{C}$.

SiC MOSFET (TW070J120B) can reduce approximately 28W power loss compared to Si IGBT, contributing to efficiency improvement of equipment.

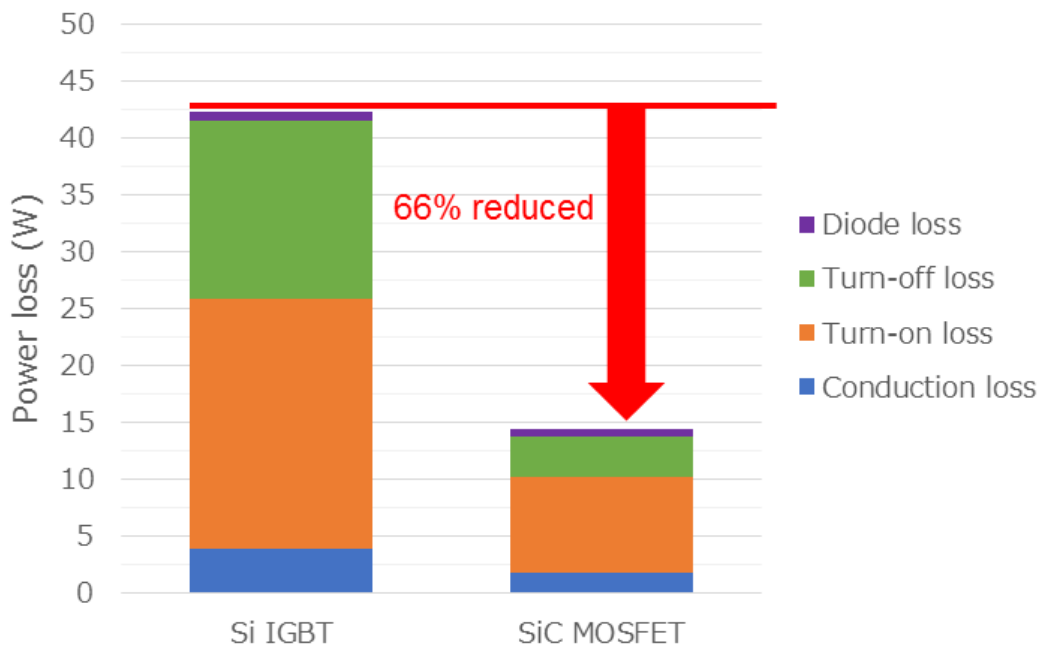


Figure 4-1 Power Loss Simulation Results

RESTRICTIONS ON PRODUCT USE

Toshiba Corporation and its subsidiaries and affiliates are collectively referred to as "TOSHIBA". Hardware, software and systems described in this document are collectively referred to as "Product".

- TOSHIBA reserves the right to make changes to the information in this document and related Product without notice.
- This document and any information herein may not be reproduced without prior written permission from TOSHIBA. Even with TOSHIBA's written permission, reproduction is permissible only if reproduction is without alteration/omission.
- Though TOSHIBA works continually to improve Product's quality and reliability, Product can malfunction or fail. Customers are responsible for complying with safety standards and for providing adequate designs and safeguards for their hardware, software and systems which minimize risk and avoid situations in which a malfunction or failure of Product could cause loss of human life, bodily injury or damage to property, including data loss or corruption. Before customers use the Product, create designs including the Product, or incorporate the Product into their own applications, customers must also refer to and comply with (a) the latest versions of all relevant TOSHIBA information, including without limitation, this document, the specifications, the data sheets and application notes for Product and the precautions and conditions set forth in the "TOSHIBA Semiconductor Reliability Handbook" and (b) the instructions for the application with which the Product will be used with or for. Customers are solely responsible for all aspects of their own product design or applications, including but not limited to (a) determining the appropriateness of the use of this Product in such design or applications; (b) evaluating and determining the applicability of any information contained in this document, or in charts, diagrams, programs, algorithms, sample application circuits, or any other referenced documents; and (c) validating all operating parameters for such designs and applications. **TOSHIBA ASSUMES NO LIABILITY FOR CUSTOMERS' PRODUCT DESIGN OR APPLICATIONS.**
- **PRODUCT IS NEITHER INTENDED NOR WARRANTED FOR USE IN EQUIPMENTS OR SYSTEMS THAT REQUIRE EXTRAORDINARILY HIGH LEVELS OF QUALITY AND/OR RELIABILITY, AND/OR A MALFUNCTION OR FAILURE OF WHICH MAY CAUSE LOSS OF HUMAN LIFE, BODILY INJURY, SERIOUS PROPERTY DAMAGE AND/OR SERIOUS PUBLIC IMPACT ("UNINTENDED USE").** Except for specific applications as expressly stated in this document, Unintended Use includes, without limitation, equipment used in nuclear facilities, equipment used in the aerospace industry, lifesaving and/or life supporting medical equipment, equipment used for automobiles, trains, ships and other transportation, traffic signaling equipment, equipment used to control combustions or explosions, safety devices, elevators and escalators, and devices related to power plant. **IF YOU USE PRODUCT FOR UNINTENDED USE, TOSHIBA ASSUMES NO LIABILITY FOR PRODUCT.** For details, please contact your TOSHIBA sales representative or contact us via our website.
- Do not disassemble, analyze, reverse-engineer, alter, modify, translate or copy Product, whether in whole or in part.
- Product shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable laws or regulations.
- The information contained herein is presented only as guidance for Product use. No responsibility is assumed by TOSHIBA for any infringement of patents or any other intellectual property rights of third parties that may result from the use of Product. No license to any intellectual property right is granted by this document, whether express or implied, by estoppel or otherwise.
- **ABSENT A WRITTEN SIGNED AGREEMENT, EXCEPT AS PROVIDED IN THE RELEVANT TERMS AND CONDITIONS OF SALE FOR PRODUCT, AND TO THE MAXIMUM EXTENT ALLOWABLE BY LAW, TOSHIBA (1) ASSUMES NO LIABILITY WHATSOEVER, INCLUDING WITHOUT LIMITATION, INDIRECT, CONSEQUENTIAL, SPECIAL, OR INCIDENTAL DAMAGES OR LOSS, INCLUDING WITHOUT LIMITATION, LOSS OF PROFITS, LOSS OF OPPORTUNITIES, BUSINESS INTERRUPTION AND LOSS OF DATA, AND (2) DISCLAIMS ANY AND ALL EXPRESS OR IMPLIED WARRANTIES AND CONDITIONS RELATED TO SALE, USE OF PRODUCT, OR INFORMATION, INCLUDING WARRANTIES OR CONDITIONS OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, ACCURACY OF INFORMATION, OR NONINFRINGEMENT.**
- Do not use or otherwise make available Product or related software or technology for any military purposes, including without limitation, for the design, development, use, stockpiling or manufacturing of nuclear, chemical, or biological weapons or missile technology products (mass destruction weapons). Product and related software and technology may be controlled under the applicable export laws and regulations including, without limitation, the Japanese Foreign Exchange and Foreign Trade Law and the U.S. Export Administration Regulations. Export and re-export of Product or related software or technology are strictly prohibited except in compliance with all applicable export laws and regulations.
- Please contact your TOSHIBA sales representative for details as to environmental matters such as the RoHS compatibility of Product. Please use Product in compliance with all applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive. **TOSHIBA ASSUMES NO LIABILITY FOR DAMAGES OR LOSSES OCCURRING AS A RESULT OF NONCOMPLIANCE WITH APPLICABLE LAWS AND REGULATIONS.**